
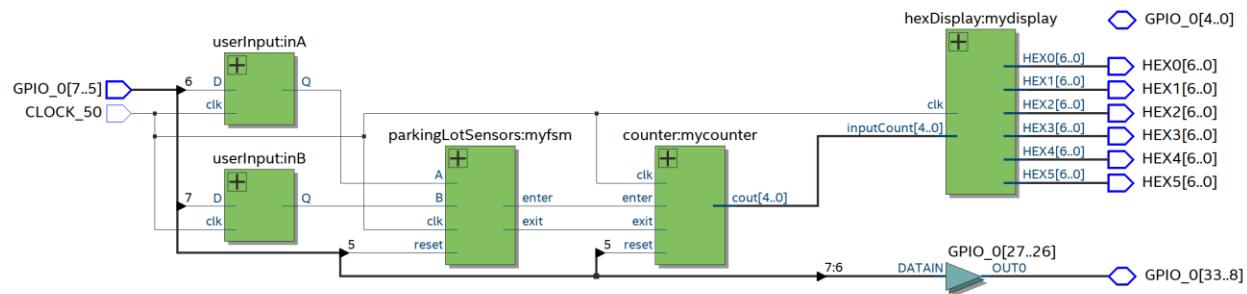



Alan Li
EE 371
January 15th, 2022
Lab 1 Report

Section 1: Procedure

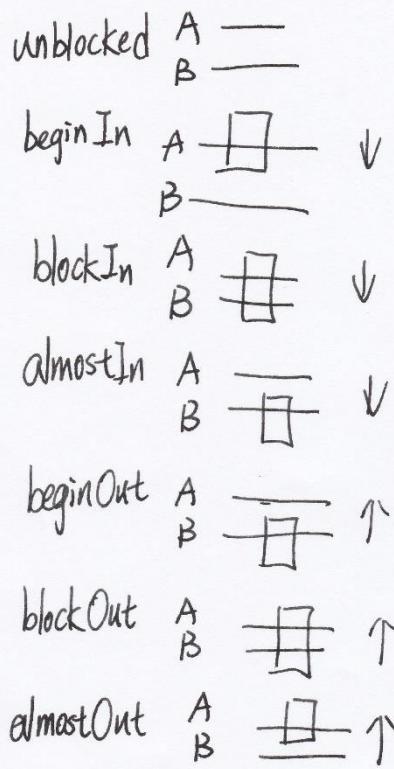



$\bar{A}\bar{B}/\text{exit}=1$

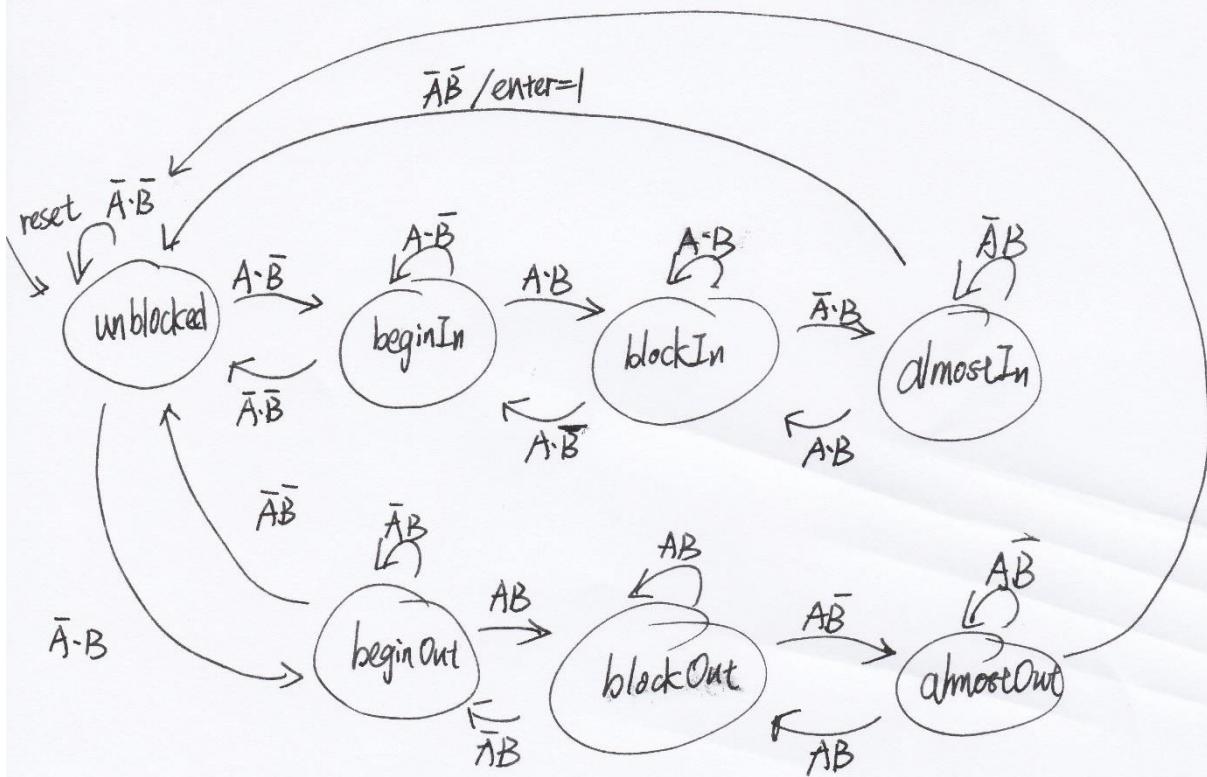

Upon reading the lab assignment, I first designed how many states there should be. There are two sensor in the system. I assume that when car enters, it will trigger sensorA first, then both sensorA and

B, then only sensorB, then none of them. So the sequence for a car entering without changing direction is 00,10,11,01,00. Similarly, the sequence for car exiting without changing direction is 00,01,11,10,00.


The reason I designed “in” and “out” in the system is that I want to tackle the changing direction issue. For example, there are two cases where only sensor A is triggered: a car just start to come in, or a car almost leave. It would be impossible for the system to decide which situation this is without adding the “in” and “out” cases. In that case, when the car comes in and then backs up after triggering sensor A, the system will recognize this and not marking it as an exit.

The rest of the system has 5 modules, userInput reduce the possibility the metastability, hexDisplay will display numbers and letters as the assignment states. The counter counts how many cars have entered or left. The parkingLotSensor is the most important part as it tells the rest of the module if there is an enter or exit signal.


Section 2 Results:

I did not design simulation for userInput as it is unnecessary.

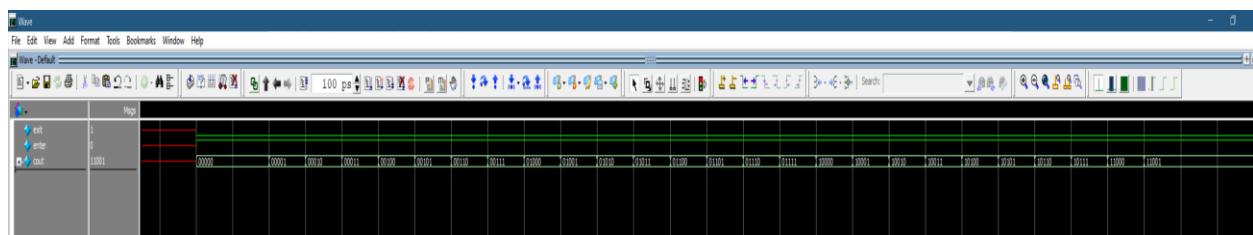For counter module I simulate enter signal for 30 times and then exit counter for 30 time. Since the parking lot only has a capacity of 25, the counter should stay at 25 and then drop to 25 and stay there.




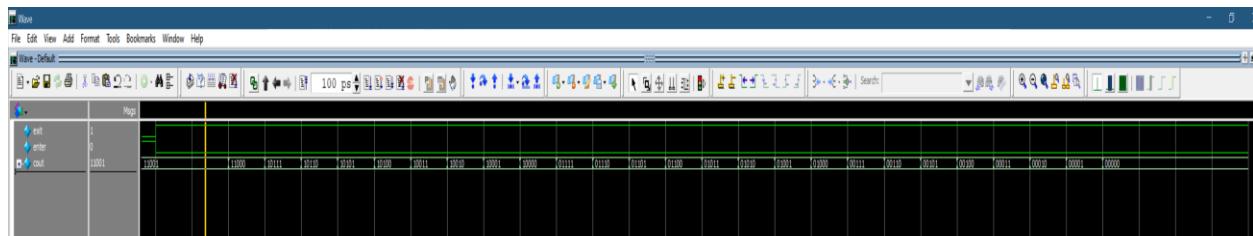The counter keeps adding up until it reached 11001(25 in decimal)




The counter decreases until reaches 0.

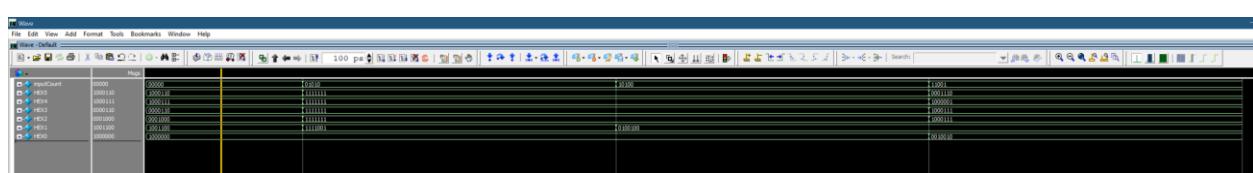For hexDisplay I simulate the counter to be at 0,10,20 and 25 respectively. And the waveform shows that the HEX displays the right number




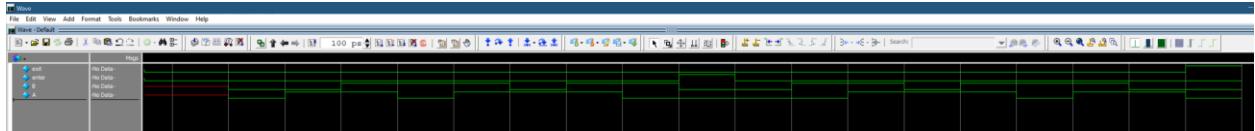For the parkingLotSensor I designed the simulator which the car will change direction multiple times and eventually enter or exit the parking lot. So, there should only be one enter and exit signal. The waveform shows the same result.



We can see the enter signal at 900ps and exit signal at 1900ps

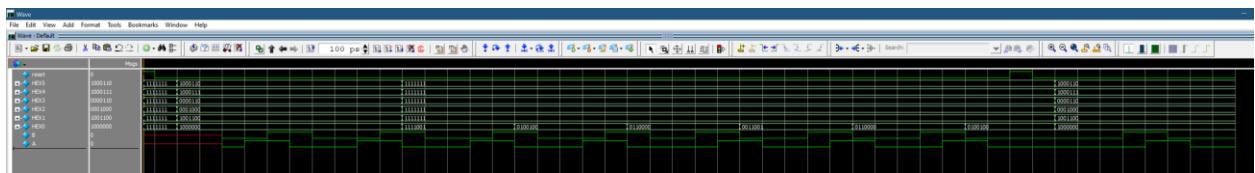For the top-level module, I simulate 4 cars enters then 3 cars exit. After that I reset the system and give one exit signal, this shouldn't happen in real life, but the system should know how to handle it. The counter will stay at zero and the hex display should display "clear0"



Overall, the system satisfies every requirement in the lab assignment. The system can handle the car changing direction issue. The system can display both numbers and letters. The counter has upper and lower limit for parking lot capacity.

Section 3: Appendix

```

1 // Alan Li
2 // 01/15/2022
3 // EE 371
4 // Lab #1
5
6 // counter takes 1-bit enter and exit as inputs and return 5-bit cout
7 // as output.
8 // The module functions as its name. When there is an enter signal, the
9 // cout increase by 1. When there is an exit signal, the cout decrease by 1.
// The range for the counter is from 0 to 25.
10
11 module counter(clk, reset, enter, exit, cout);
12     input logic clk, reset, enter, exit;
13     output logic [4:0] cout;
14     logic [4:0] ps, ns;
15
16     // Each decimal from 0 to 25 has been assigned with a 5-bit binary
17     // number.
18     parameter [4:0] zero = 5'b0,
19         one = 5'b1,
20         two = 5'b10,
21         three = 5'b11,
22         four = 5'b100,
23         five = 5'b101,
24         six = 5'b110,
25         seven = 5'b111,
26         eight = 5'b1000,
27         nine = 5'b1001,
28         ten = 5'b1010,
29         eleven = 5'b1011,
30         twelve = 5'b1100,
31         thirteen = 5'b1101,
32         fourteen = 5'b1110,
33         fifteen = 5'b1111,
34         sixteen = 5'b10000,
35         seventeen = 5'b10001,
36         eighteen = 5'b10010,
37         nineteen = 5'b10011,
38         twenty = 5'b10100,
39         twentyone = 5'b10101,
40         twentytwo = 5'b10110,
41         twentythree = 5'b10111,
42         twentyfour = 5'b11000,
43         twentyfive = 5'b11001;
44
45     // 25 states for the counter. Each state represent a different
46     // number.
47     // When there is a enter signal, the counter goes to next state
48     // which the number increase by one and vice versa.
49     // At state 0, if there is another exit signal(which should not
50     // happen in reality), the state will stay at zero.
51     // At state 25, if there is another enter signal, the state will
52     // stay at 25.
53     case(ps)
54         zero: if(enter)           ns = one;
55             else                  ns = zero;
56         one:  if(enter)           ns = two;

```

```

52           else if(exit)      ns = zero;
53           else               ns = one;
54       two: if(enter)        ns = three;
55           else if(exit)     ns = one;
56           else               ns = two;
57   three:if(enter)        ns = four;
58           else if(exit)    ns = two;
59           else               ns = three;
60   four: if(enter)         ns = five;
61           else if(exit)   ns = three;
62           else               ns = four;
63
64  /*
65   five: if(exit)
66       else
67 */
68
69
70   five: if(enter)        ns = six;
71       else if(exit)     ns = four;
72       else               ns = five; // for lab design purpose
73
74   six: if(enter)          ns = seven;
75       else if(exit)    ns = five;
76       else               ns = six;
77   seven:if(enter)        ns = eight;
78       else if(exit)   ns = six;
79       else               ns = seven;
80   eight:if(enter)        ns = nine;
81       else if(exit)  ns = seven;
82       else               ns = eight;
83   nine: if(enter)         ns = ten;
84       else if(exit)   ns = eight;
85       else               ns = nine;
86   ten:  if(enter)          ns = eleven;
87       else if(exit)  ns = nine;
88       else               ns = ten;
89   eleven:if(enter)       ns = twelve;
90       else if(exit)   ns = ten;
91       else               ns = eleven;
92   twelve:if(enter)       ns = thirteen;
93       else if(exit)  ns = eleven;
94       else               ns = twelve;
95   thirteen:if(enter)      ns = fourteen;
96       else if(exit)   ns = twelve;
97       else               ns = thirteen;
98   fourteen: if(enter)      ns = fifteen;
99       else if(exit)  ns = thirteen;
100      else               ns = fourteen;
101   fifteen:if(enter)       ns = sixteen;
102       else if(exit)  ns = fourteen;
103       else               ns = fifteen;
104   sixteen: if(enter)      ns = seventeen;
105       else if(exit)  ns = fifteen;
106       else               ns = sixteen;
107   seventeen:if(enter)      ns = eighteen;
108       else if(exit)  ns = sixteen;
109       else               ns = seventeen;

```

```

110      eighteen:if(enter)      ns = nineteen;
111          else if(exit)    ns = seventeen;
112          else             ns = eighteen;
113      nineteen:if(enter)    ns = twenty;
114          else if(exit)    ns = eighteen;
115          else             ns = nineteen;
116      twenty:if(enter)     ns = twentyone;
117          else if(exit)   ns = nineteen;
118          else             ns = twenty;
119      twentyone:if(enter)   ns = twentytwo;
120          else if(exit)   ns = twenty;
121          else             ns = twentyone;
122      twentytwo:if(enter)  ns = twentythree;
123          else if(exit)  ns = twentyone;
124          else             ns = twentytwo;
125      twentythree:if(enter) ns = twentyfour;
126          else if(exit)  ns = twentytwo;
127          else             ns = twentythree;
128      twentyfour:if(enter) ns = twentyfive;
129          else if(exit)  ns = twentythree;
130          else             ns = twentyfour;
131      twentyfive:if(exit) ns = twentyfour;
132          else             ns = twentyfive;
133      endcase
134  end
135
136 // when reset is pressed, the counter will reset to state 0.
137 always @(posedge clk) begin
138     if(reset) begin
139         ps <= zero;
140     end
141     else begin
142         cout <= ps;
143         ps <= ns;
144     end
145 end
146 endmodule
147
148 // counter_testbench tests all expected behavior that the parking lot
149 // occupancy counter system in the lab may encounter
150 module counter_testbench();
151     logic clk, reset, enter, exit;
152     logic [4:0]cout;
153
154     counter dut (.clk(clk), .reset(reset), .enter(enter), .exit(exit), .
155     cout(cout));
156
157     parameter CLOCK_PERIOD = 100;
158
159     initial begin
160         clk <= 0;
161         forever #(CLOCK_PERIOD/2) clk <= ~clk;
162     end
163
164     // 30 cars enters, the counter will reach 25 and stay there
165     // 30 cars exit(for simulation), the counter will reach 0 and stay
166     // there
167     initial begin

```

```
165      reset <= 1;          @(posedge clk);
166      reset <= 0;          @(posedge clk);
167      enter <= 1; exit <= 0; repeat(30) @(posedge clk);
168      enter <= 0; exit <= 1; repeat(30) @(posedge clk);
169      $stop;
170  end
171 endmodule
172
173
174
```

```

1 // Alan Li
2 // 01/15/2022
3 // EE 371
4 // Lab #1
5
6 // DE1_Soc takes 34-bit GPIO_0 and return 1-bit enterIndicator and
7 // exitIndicator, 5-bit countIndicator and inputA, inputB
8 // This serves as the top-level module for the parking lot occupancy
9 // counter system
10
11 module DE1_Soc(CLOCK_50, GPIO_0, HEX5, HEX4, HEX3, HEX2, HEX1, HEX0);
12     // GPIO_0[5] is connected to the reset switch, GPIO_0[6] is
13     // connected to the sensorA switch, GPIO_0[7] is connected to the sensorB
14     // switch
15     inout logic [33:0] GPIO_0;
16     input logic CLOCK_50;
17     output logic [6:0] HEX5, HEX4, HEX3, HEX2, HEX1, HEX0;
18     logic enterIndicator, exitIndicator;
19     logic [4:0] countIndicator;
20     logic inputA, inputB;
21
22     assign GPIO_0[26] = GPIO_0[6]; // when switch A(sensor A) is
23     // enabled/triggered the corresponding LED turns on
24     assign GPIO_0[27] = GPIO_0[7]; // when switch B(sensor B) is
25     // enabled/triggered the corresponding LED turns on
26
27     // userInput inA and inB takes GPIO[6] and GPIO[7] as input
28     // parameters and return Q as inputA and inputB respectively
29     userInput inA (.clk(CLOCK_50), .D(GPIO_0[6]), .Q(inputA));
30     userInput inB (.clk(CLOCK_50), .D(GPIO_0[7]), .Q(inputB));
31
32     // parkingLotSensors my fsm takes CLOCK_50 as clk, GPIO[5], inputA,
33     // input B as parameters to reset, A, B
34     // and returns enter and exit as enterIndicator and exitIndicator
35     // respectively
36     parkingLotSensors my fsm (.clk(CLOCK_50), .reset(GPIO_0[5]), .A(inputA),
37     .B(inputB), .enter(enterIndicator), .exit(exitIndicator));
38
39     // counter mycounter takes CLOCK_50 as clk, GPIO_0[5],
40     // enterIndicator and exitIndicator as reset, enter and exit
41     // it returns enter, exit and cout as countIndicator[4:0]
42     counter mycounter (.clk(CLOCK_50), .reset(GPIO_0[5]), .enter(
43         enterIndicator), .exit(exitIndicator), .cout(countIndicator[4:0]));
44
45     // hexDisplay mydisplay takes CLOCK_50 as clk, countIndicator[4:0]
46     // as inputCount
47     // and returns HEX5, HEX4, HEX3, HEX2, HEX1, HEX0 as HEX5, HEX4,
48     // HEX3, HEX2, HEX1, HEX0 respectively
49     hexDisplay mydisplay (.clk(CLOCK_50), .inputCount(countIndicator[4:0]),
50     .HEX5(HEX5), .HEX4(HEX4), .HEX3(HEX3), .HEX2(
51     HEX2), .HEX1(HEX1), .HEX0(HEX0));
52 endmodule
53
54 // DE1_Soc_testbench tests all expected behavior that the parking lot

```

```

occupancy counter system in the lab may encounter
43 module DE1_SoC_testbench();
44
45     logic clk, reset, A, B;
46     logic [6:0] HEX5, HEX4, HEX3, HEX2, HEX1, HEX0;
47
48     DE1_SoC dut (.CLOCK_50(CLOCK_50), .GPIO_0(GPIO_0),
49                 .HEX5(HEX5), .HEX4(HEX4), .HEX3(HEX3), .HEX2(
50                 HEX2), .HEX1(HEX1), .HEX0(HEX0));
51
52     //set up the clock.
53     parameter CLOCK_PERIOD = 100;
54
55     initial begin
56         clk <= 0;
57         forever #(CLOCK_PERIOD/2) clk <= ~clk;
58     end
59
60     initial begin
61         reset <= 1;           @(posedge clk); // cycle through car entering
62         reset <= 0;           @(posedge clk);
63
64         {A,B} <= 2'b00;      @(posedge clk);
65         {A,B} <= 2'b10;      @(posedge clk);
66         {A,B} <= 2'b11;      @(posedge clk);
67         {A,B} <= 2'b01;      @(posedge clk);
68         {A,B} <= 2'b00;      @(posedge clk);
69
70         {A,B} <= 2'b00;      @(posedge clk);
71         {A,B} <= 2'b10;      @(posedge clk);
72         {A,B} <= 2'b11;      @(posedge clk);
73         {A,B} <= 2'b01;      @(posedge clk);
74         {A,B} <= 2'b00;      @(posedge clk);
75
76         {A,B} <= 2'b00;      @(posedge clk);
77         {A,B} <= 2'b10;      @(posedge clk);
78         {A,B} <= 2'b11;      @(posedge clk);
79         {A,B} <= 2'b01;      @(posedge clk);
80         {A,B} <= 2'b00;      @(posedge clk);
81
82         {A,B} <= 2'b00;      @(posedge clk);
83         {A,B} <= 2'b10;      @(posedge clk);
84         {A,B} <= 2'b11;      @(posedge clk);
85         {A,B} <= 2'b01;      @(posedge clk);
86         {A,B} <= 2'b00;      @(posedge clk);
87
88         {A,B} <= 2'b00;      @(posedge clk);
89         {A,B} <= 2'b01;      @(posedge clk);
90         {A,B} <= 2'b11;      @(posedge clk);
91         {A,B} <= 2'b10;      @(posedge clk);
92         {A,B} <= 2'b00;      @(posedge clk);
93
94         {A,B} <= 2'b00;      @(posedge clk);
95         {A,B} <= 2'b01;      @(posedge clk);
96         {A,B} <= 2'b11;      @(posedge clk);
97         {A,B} <= 2'b10;      @(posedge clk);
98
// 4 cars entered

```

```
99      {A,B} <= 2'b00;    @(posedge clk);
100
101     {A,B} <= 2'b00;    @(posedge clk);
102     {A,B} <= 2'b01;    @(posedge clk);
103     {A,B} <= 2'b11;    @(posedge clk);
104     {A,B} <= 2'b10;    @(posedge clk);
105     {A,B} <= 2'b00;    @(posedge clk);
106
107     reset <= 1;        @(posedge clk);
108     reset <= 0;        @(posedge clk);
109
110
111     {A,B} <= 2'b00;    @(posedge clk);
112     {A,B} <= 2'b01;    @(posedge clk);
113     {A,B} <= 2'b11;    @(posedge clk);
114     {A,B} <= 2'b10;    @(posedge clk);
115     {A,B} <= 2'b00;    @(posedge clk);
116
117     $stop;
118 end
119 endmodule
120
```

```

1  // Alan Li
2  // 01/15/2022
3  // EE 371
4  // Lab #1
5
6  // hexDisplay takes 5-bit inputCount as inputs and return 7-bits HEX5,
7  // HEX4, HEX3, HEX2, HEX1, HEX0 as output.
8  // Upon start, the HEX display will display "clear0", when enter signal
9  // is given, the HEX display the counter on HEX1 and HEX0. The counter
10 // will keep adding up until reach 25.
11 // Then the hex display will display "FULL25".
12 // If the counter reach 0, the hex display will display "clear0" as
13 // there is no car in the parking lot
14
15 module hexDisplay(clk, inputCount, HEX5, HEX4, HEX3, HEX2, HEX1, HEX0);
16   input clk;
17   input logic [4:0] inputCount;
18   output logic [6:0] HEX5, HEX4, HEX3, HEX2, HEX1, HEX0;
19
20   // 7-bit parameter for the display to display different numbers or
21   // characters
22   // 6543210
23   parameter [6:0] zero = 7'b1000000,
24     one = 7'b1111001,
25     two = 7'b0100100,
26     three = 7'b0110000,
27     four = 7'b0011001,
28     five = 7'b0010010,
29     six = 7'b0000010,
30     seven = 7'b1111000,
31     eight = 7'b0000000,
32     nine = 7'b0011000,
33     F = 7'b0001110, //FULL
34     U = 7'b1000001,
35     L = 7'b1000111,
36
37
38   // The hex are driven off upon start.
39   // The hex will display counters when enter or exit signal is given
40   // when the counter is 0, it will display "clear0". When full it
41   // will display "full25"
42   always_comb begin
43     HEX5 = blk;
44     HEX4 = blk;
45     HEX3 = blk;
46     HEX2 = blk;
47     HEX1 = blk;
48     HEX0 = blk;
49     case(inputCount)
50       0: begin HEX5 = C; HEX4 = L; HEX3 = E; HEX2 = A; HEX1 = R; HEX0
51       = zero; end
           1: begin HEX5 = blk; HEX4 = blk; HEX3 = blk; HEX2 = blk; HEX1 =

```

```

52      blk; HEX0 = one; end
53          2: begin HEX5 = blk; HEX4 = blk; HEX3 = blk; HEX2 = blk; HEX1 =
54              blk; HEX0 = two; end
55                  3: begin HEX5 = blk; HEX4 = blk; HEX3 = blk; HEX2 = blk; HEX1 =
56                      blk; HEX0 = three; end
57                          4: begin HEX5 = blk; HEX4 = blk; HEX3 = blk; HEX2 = blk; HEX1 =
58                              blk; HEX0 = four; end
59                                  5: begin HEX5 = F; HEX4 = U; HEX3 = L; HEX2 = L; HEX1 = blk;
60                                      HEX0 = five; end // for demo purpose
61
62      //5: begin HEX5 = blk; HEX4 = blk; HEX3 = blk; HEX2 = blk; HEX1 =
63          HEX1 = blk; HEX0 = five; end
64          6: begin HEX5 = blk; HEX4 = blk; HEX3 = blk; HEX2 = blk; HEX1 =
65              blk; HEX0 = six; end
66              7: begin HEX5 = blk; HEX4 = blk; HEX3 = blk; HEX2 = blk; HEX1 =
67                  blk; HEX0 = seven; end
68                  8: begin HEX5 = blk; HEX4 = blk; HEX3 = blk; HEX2 = blk; HEX1 =
69                      blk; HEX0 = eight; end
70                      9: begin HEX5 = blk; HEX4 = blk; HEX3 = blk; HEX2 = blk; HEX1 =
71                          blk; HEX0 = nine; end
72                          10: begin HEX5 = blk; HEX4 = blk; HEX3 = blk; HEX2 = blk; HEX1 =
73                              one; HEX0 = zero; end
74                              11: begin HEX5 = blk; HEX4 = blk; HEX3 = blk; HEX2 = blk; HEX1 =
75                                  one; HEX0 = one; end
76                                  12: begin HEX5 = blk; HEX4 = blk; HEX3 = blk; HEX2 = blk; HEX1 =
77                                      one; HEX0 = two; end
78                                      13: begin HEX5 = blk; HEX4 = blk; HEX3 = blk; HEX2 = blk; HEX1 =
79                                          one; HEX0 = three; end
80                                          14: begin HEX5 = blk; HEX4 = blk; HEX3 = blk; HEX2 = blk; HEX1 =
81                                              one; HEX0 = four; end
82                                              15: begin HEX5 = blk; HEX4 = blk; HEX3 = blk; HEX2 = blk; HEX1 =
83                                                  one; HEX0 = five; end
84                                              16: begin HEX5 = blk; HEX4 = blk; HEX3 = blk; HEX2 = blk; HEX1 =
85                                                  one; HEX0 = six; end
86                                                  17: begin HEX5 = blk; HEX4 = blk; HEX3 = blk; HEX2 = blk; HEX1 =
87                                                      one; HEX0 = seven; end
88                                                      18: begin HEX5 = blk; HEX4 = blk; HEX3 = blk; HEX2 = blk; HEX1 =
89                                                          one; HEX0 = eight; end
90                                                          19: begin HEX5 = blk; HEX4 = blk; HEX3 = blk; HEX2 = blk; HEX1 =
91                                                              one; HEX0 = nine; end
92                                                              20: begin HEX5 = blk; HEX4 = blk; HEX3 = blk; HEX2 = blk; HEX1 =
93                      two; HEX0 = zero; end
94                      21: begin HEX5 = blk; HEX4 = blk; HEX3 = blk; HEX2 = blk; HEX1 =
95                          two; HEX0 = one; end
96                          22: begin HEX5 = blk; HEX4 = blk; HEX3 = blk; HEX2 = blk; HEX1 =
97                              two; HEX0 = two; end
98                              23: begin HEX5 = blk; HEX4 = blk; HEX3 = blk; HEX2 = blk; HEX1 =
99                                  two; HEX0 = three; end
100                                  24: begin HEX5 = blk; HEX4 = blk; HEX3 = blk; HEX2 = blk; HEX1 =
101                                      two; HEX0 = four; end
102                                      25: begin HEX5 = F; HEX4 = U; HEX3 = L; HEX2 = L; HEX1 = two;
103                                          HEX0 = five; end
104
105      endcase
106  end
107
108 endmodule
109
110 // counter_testbench tests all expected behavior that the parking lot

```

```
occupancy counter system in the lab may encounter
84 module hexDisplay_testbench();
85   logic clk;
86   logic [4:0] inputCount;
87   logic [6:0] HEX5, HEX4, HEX3, HEX2, HEX1, HEX0;
88
89   hexDisplay dut (.clk(clk), .inputCount(inputCount), .HEX5(HEX5), .
90   HEX4(HEX4), .HEX3(HEX3), .HEX2(HEX2), .HEX1(HEX1), .HEX0(HEX0));
91
92   parameter CLOCK_PERIOD = 100;
93
94   initial begin
95     clk <= 0;
96     forever #(CLOCK_PERIOD/2) clk <= ~clk;
97   end
98
99   initial begin
100     inputCount <= 0; @(posedge clk);
101     inputCount <= 10; @(posedge clk);
102     inputCount <= 20; @(posedge clk);
103     inputCount <= 25; @(posedge clk);
104     $stop;
105   end
106 endmodule
```

```

1 // Alan Li
2 // 01/15/2022
3 // EE 371
4 // Lab #1
5
6 // parkingLotSensors takes in 1-bit A, B and clk as inputs and return
7 // 1-bit enter and exit as outputs.
8 module parkingLotSensors(clk, reset, A, B, enter, exit);
9   input logic A, B, clk, reset;
10  output logic enter, exit;
11
12  // States
13  enum {unblocked, beginIn, blockIn, almostIn, beginout, blockout,
14  almostOut} ps, ns;
15
16  // The parking lot sensor can have six cases as list below. beginIn,
17  blockin and almostIn are pairs with almostOut, blockout and beginOut.
18  // Assume the entrance is north-south direction. If car is entering
19  from North, it will trigger sensor A first.
20  // If car is exiting from South it will trigger sensor B first.
21  // For example, beginIn and almost out both indicate that only
22  sensorA is blocked, they only differences is that beginIn means the car
23  is going in the south direction and almostOut is car going north.
24  // This "case pair" is designed to tackle car changing direction
25  issue.
26  always_comb
27  begin
28    enter = 0;
29    exit = 0;
30
31    case(ps)
32
33      unblocked:
34        enter
35        if (A & ~B)          ns = beginIn;    // car begin to
36        exit
37        else if (~A & B)     ns = beginout;   // car begin to
38        else if (~A & ~B)    ns = unblocked; // impossible
39        else                  ns = unblocked; // nothing happens
40
41      beginIn:
42        halfway entering
43        if (A & B)          ns = blockIn;   // car is
44        enters then back up
45        else if (~A & ~B)   ns = unblocked; // car just
46        else                  ns = beginIn;   // impossible
47        move
48
49      blockIn:
50        enters (trigger both sensors)
51        if (~A & B)         ns = almostIn; // car almost
52        else if (A & ~B)    ns = beginIn;   // car backs up
53        // else if (A & B)    ns = blockIn; // impossible
54        else                  ns = blockIn;   // car does not
55        move
56
57
58
59
60
61
62
63
64
65
66
67
68
69
70
71
72
73
74
75
76
77
78
79
80
81
82
83
84
85
86
87
88
89
90
91
92
93
94

```

```

45      almostIn:
46          if (~A & ~B)
47              begin
48                  ns = unblocked;    // car enters
49                  enter = 1;
50                  exit = 0;
51          end
52      else if (A % B)           ns = blockIn;    // car backs up
53      // else if (~A & B)       ns = almostIn;   // impossible
54      else                      ns = almostIn;   // car does not
55      move
56
57          beginOut:
58              if (A & B)           ns = blockout;   // car is
59              else if (~A & ~B)  ns = unblocked;  // car backs up
60              // else if (~A & B) ns = beginOut;  // impossible
61              else                  ns = beginOut;  // car does not
62      move
63
64          blockout:
65              if (A & ~B)           ns = almostOut; // car almost
66      exits (trigger both sensors)
67              else if (~A & B)  ns = beginOut; // car backs up
68              // else if (A & B)  ns = blockout; // impossible
69              else                  ns = blockout; // car does not
70      move
71
72          almostOut:
73              if (~A & ~B)
74                  begin
75                      ns = unblocked;
76                      enter = 0;
77                      exit = 1;
78                  end
79              else if (A & B)           ns = blockout; // car backs up
80              // else if (A & ~B)     ns = almostOut; // impossible
81              else                  ns = almostOut; // car does not
82      move
83
84          /*
85      default:
86          begin
87              enter = 0;
88              exit = 0;
89          end
90      */
91      endcase
92  end
93
94  // if reset, the parking lot sensor goes to unblocked case
95  always_ff @(posedge clk)
96      begin
97          if (reset)
98              ps <= unblocked;
99          else ps <= ns;
100     end

```

```

97  endmodule
98
99 // parkingLotSensor_testbench tests all expected behavior that the
100 // parking lot occupancy counter system in the lab may encounter
101 module parkingLotSensor_testbench();
102   logic clk, reset, A, B, enter, exit;
103
104   parkingLotSensors dut (.clk(clk), .reset(reset), .A(A), .B(B), .enter
105   (enter), .exit(exit));
106
107   parameter CLOCK_PERIOD = 100;
108
109   initial begin
110     clk <= 0;
111     forever #(CLOCK_PERIOD/2) clk <= ~clk;
112   end
113
114 // I have already simulate the case where car enters and exits
115 // without changing directions in DE1_SoC
116 // For this testbench I will simulate the case where the car changes
117 // direction multiple times
118 initial begin
119   reset <= 1;           @(posedge clk);
120   reset <= 0;           @(posedge clk);
121   {A, B} <= 2'b00;      @(posedge clk);
122   {A, B} <= 2'b10;      @(posedge clk);
123   {A, B} <= 2'b11;      @(posedge clk);
124   {A, B} <= 2'b01;      @(posedge clk);
125   {A, B} <= 2'b10;      @(posedge clk); // simulation for car enters
126
127   {A, B} <= 2'b00;      @(posedge clk);
128   {A, B} <= 2'b01;      @(posedge clk);
129   {A, B} <= 2'b11;      @(posedge clk);
130   {A, B} <= 2'b10;      @(posedge clk);
131   {A, B} <= 2'b11;      @(posedge clk);
132   {A, B} <= 2'b01;      @(posedge clk);
133   {A, B} <= 2'b11;      @(posedge clk);
134   {A, B} <= 2'b10;      @(posedge clk);
135   {A, B} <= 2'b00;      @(posedge clk); // simulation for car exits
136   $stop;
137 end
138 endmodule
139
140
141
142

```

```
1 // Alan Li
2 // 01/15/2022
3 // EE 371
4 // Lab #1
5
6 // userInput take 1-bit D as user input and return Q as output
7 // This module utilize two DFF to reduce the possibility of
8 // metastability by adding latency
9 module userInput(clk, D, Q);
10    input clk, D;
11    output logic Q;
12    logic temp;
13
14    always_ff @(posedge clk) begin
15        temp <= D;
16        Q <= temp;
17    end
18
19 endmodule
```